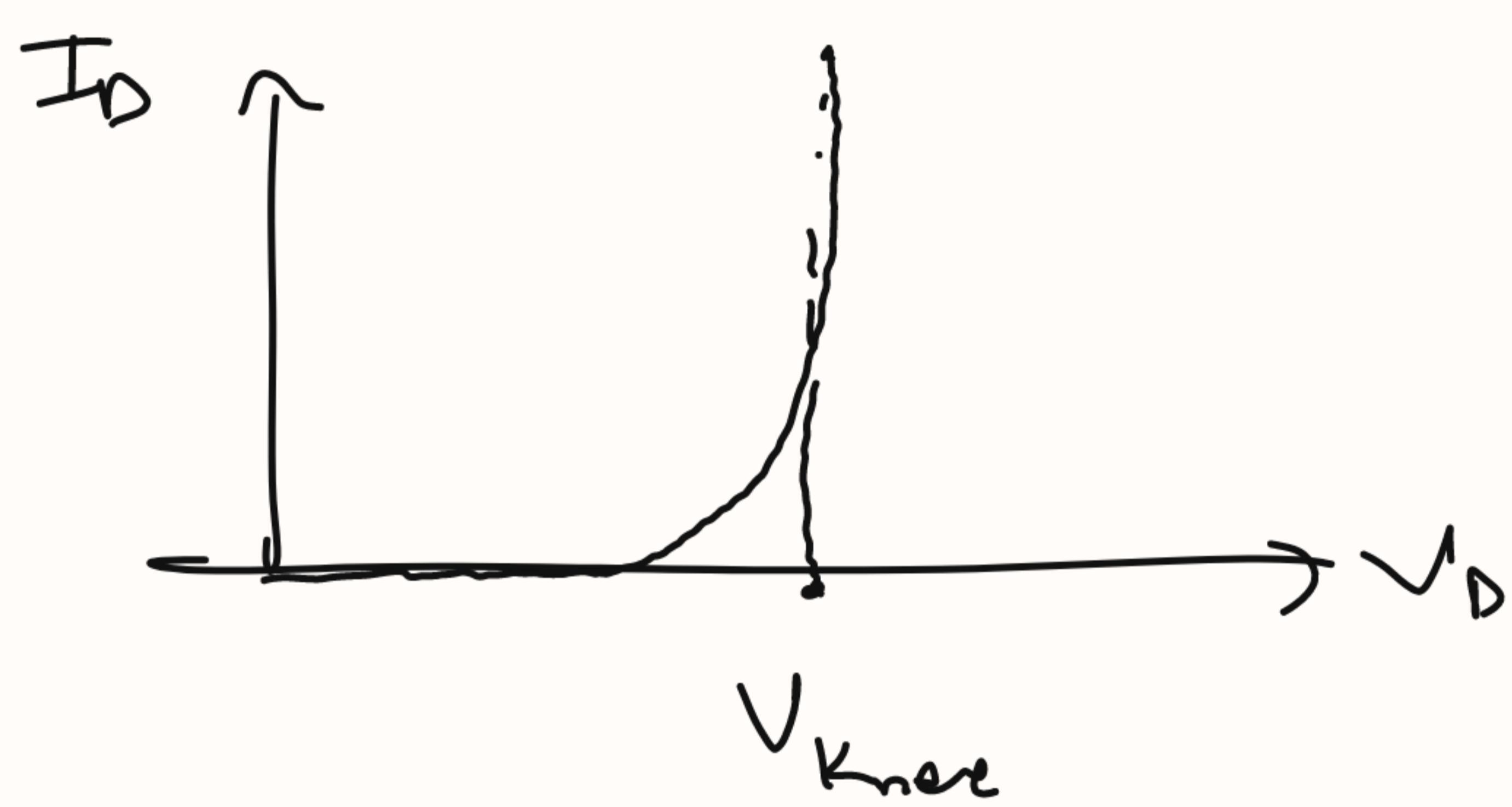


Voltage Mode BGR

① The basic Idea:

→ The basic concept behind a BGR is, we need a reference voltage / current which is constant with temperature. And the first thing that comes in mind is a diode. Let's look at the characteristics of a diode,



→ As we can see that I_D does not vary much with respect to voltage around V_{Knee} . Let's analyze the diode through its equations.

$$I_D \approx I_S e^{\frac{V_{be}}{V_T}} ; \text{ In forward bias.}$$

$$\therefore V_{be} = V_T \ln \left(\frac{I_D}{I_S} \right)$$

$$\rightarrow V_{be} = \frac{k_b T}{q} \ln \left(\frac{I_D}{I_S} \right)$$

$$\rightarrow \text{Now, } I_s \propto n k_B T n_i^2$$

$$\rightarrow n \propto T^{-m}, \quad n_i^2 \propto T^3 e^{-E_g/k_B T}$$

$$\therefore I_s \propto T^{(4-m)} e^{-E_g/k_B T}$$

$$\therefore \text{Let } I_s = C e^{-E_g/k_B T} T^{(4-m)}$$

$$\therefore V_{be} = \frac{k_B T}{I} \ln \left(\frac{I_0}{C e^{-E_g/k_B T} T^{(4-m)}} \right)$$

$$\therefore V_{be} = \frac{k_B T}{I} \left\{ \ln(I_0) - \ln(C) + \frac{E_g}{k_B T} - (4-m) \ln(T) \right\}$$


$$\therefore V_{be} = \frac{1}{I} \left\{ k_B T \ln(I_0) - k_B T \ln(C) + E_g - (4-m) k_B T \ln(T) \right\}$$

$$\therefore V_{be} = \frac{1}{I} \left\{ k_B T \ln \left(\frac{I_0}{C} \right) - (4-m) k_B T \ln(T) + E_g \right\}$$


$$\rightarrow E_g = E_{g0} - \alpha T$$

$$\therefore V_{be} = \frac{1}{I} \left\{ k_B T \ln \left(\frac{I_0}{C} \right) - (4-m) k_B T \ln(T) + E_{g0} - \alpha T \right\} - \textcircled{1}$$

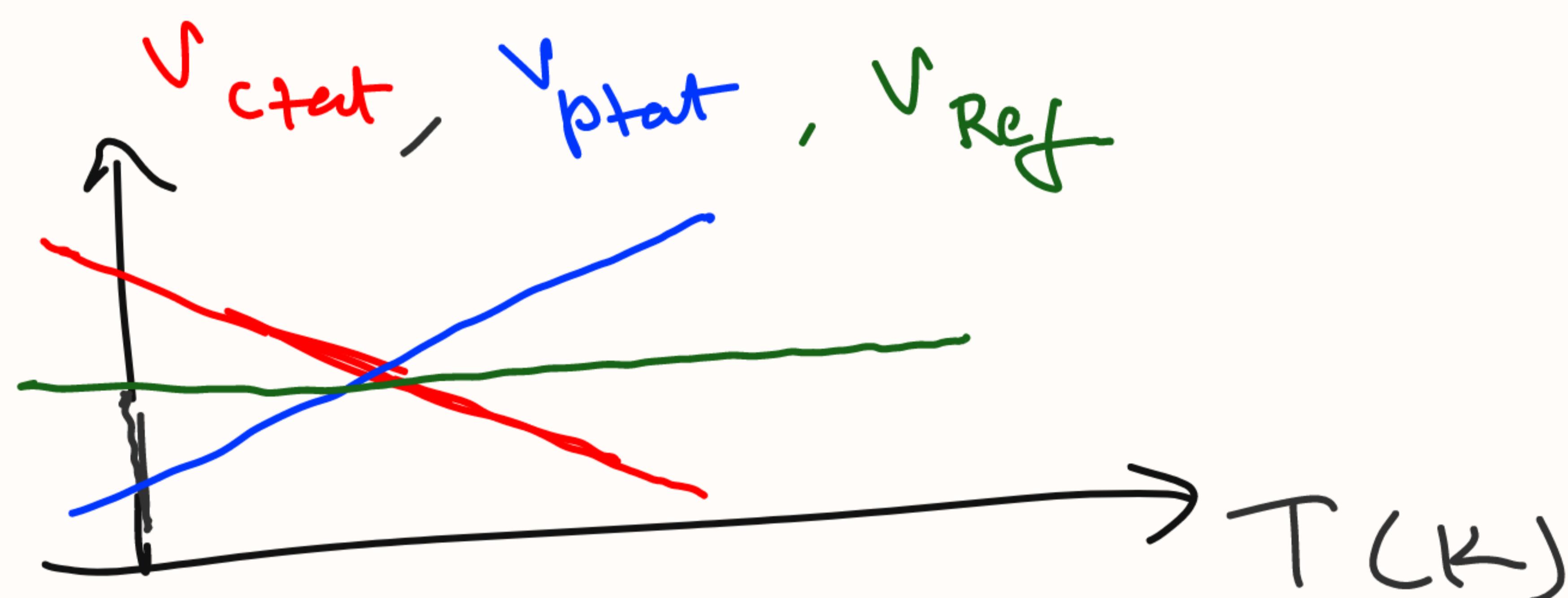- Clearly V_{be} is a CTAT (Complementary with absolute temperature) i.e. V_{be} reduces as temperature increases.
- Also note that it is mostly a linear fashion of decrease with some amount of non-linearity.
- Now to get a constant voltage reference the idea is to add a PTAT voltage (Proportional to absolute temperature) which has same slope.



⇒ Schematic :

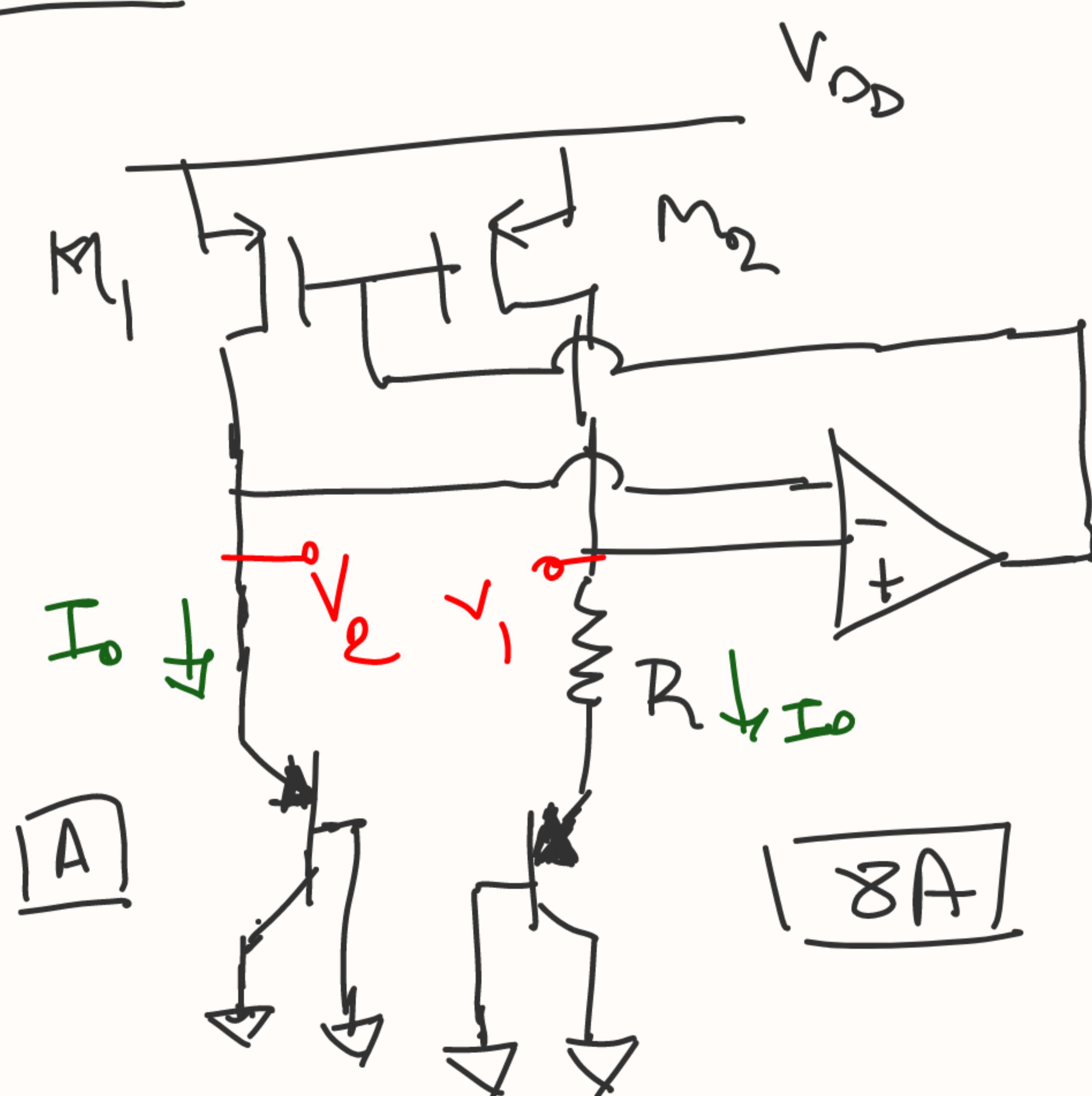

→ Note that due to op-amp $V_1 = V_2$. Also V_{GS} of M_1 & M_2 are same so current flowing through both the branch is same.

→ Now, $V_2 = V_T \ln\left(\frac{I_o}{I_s}\right)$, and $V_1 = V_T \ln\left(\frac{I_o}{8I_s}\right) + I_o R$

→ Thus let $V_d = \text{difference voltage be defined as}$


$$V_d = V_1 - V_2 \quad \text{for } V_d = 0, \text{ we get}$$

$$V_T \ln\left(\frac{I_o}{I_s}\right) = V_T \ln\left(\frac{I_o}{8I_s}\right) + I_o R$$

$$\therefore I_o R = V_T \ln(8)$$

$$\therefore I_o = \frac{V_T \ln(8)}{R} = \frac{kT}{I} \frac{\ln(8)}{R} \quad \text{--- (2)}$$


→ Thus I_o is a PTAT current.

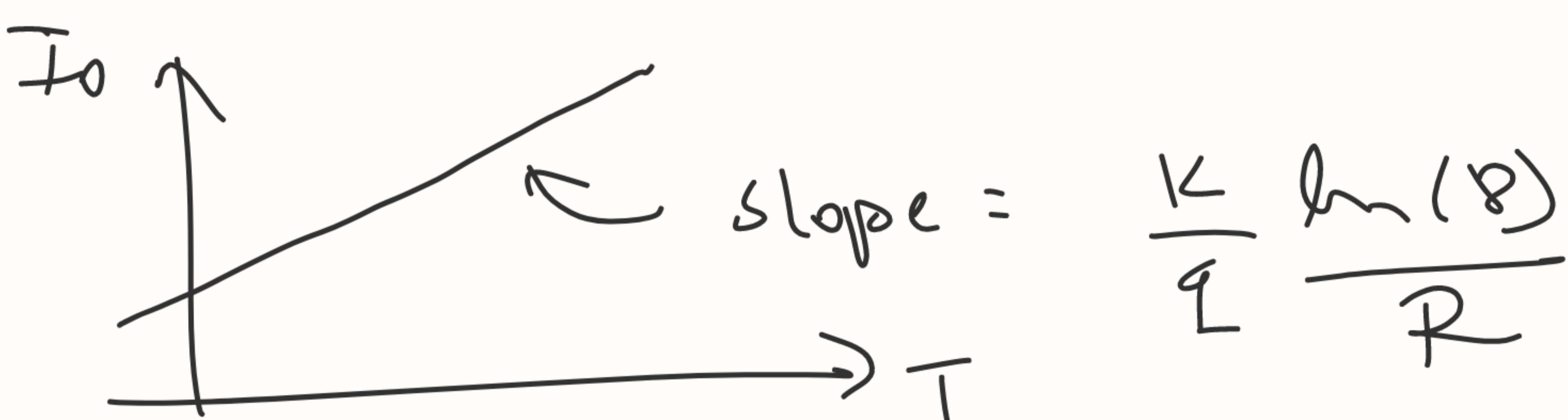

→ Now this PTAT current passes through our diode (i.e. diode connected BJT's), even though our analysis of V_{BE} to be a CTAT voltage for a constant current one can substitute PTAT I_o in the equation and still

the nature of diode voltage will be CTAT.

→ Plot of V_1, V_2 & V_d vs I_o

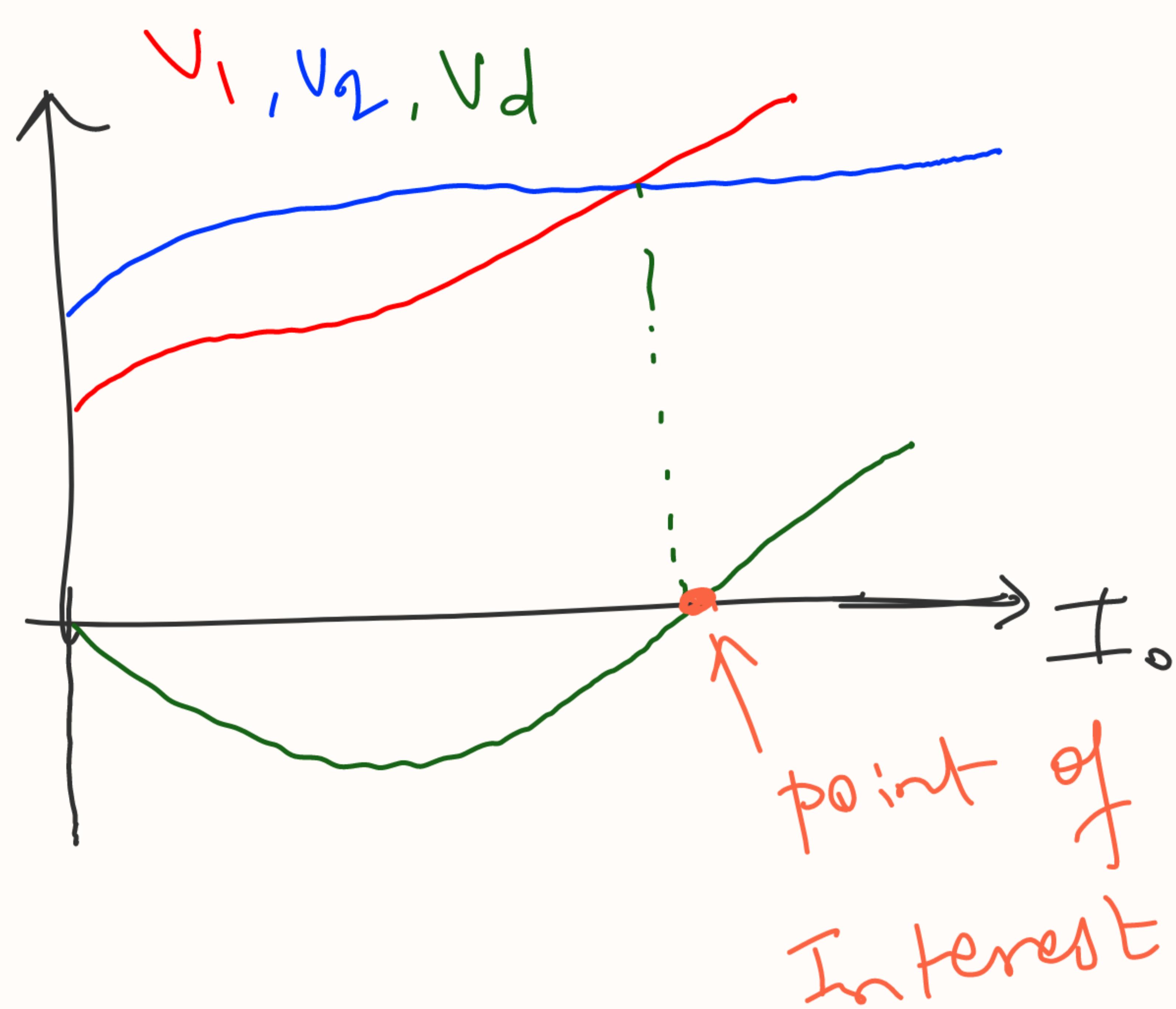

→ As for a PTAT current we need $V_d = 0$ and this happens at a particular I_o , i.e. $I_o = \frac{V_t \ln(8)}{R}$.

→ Now for feedback we can see that if


• $V_d > 0 \Rightarrow$ we must decrease I_o .

• $V_d < 0 \Rightarrow$ we must increase I_o .

→ As $V_d = V_1 - V_2$, thus V_1 must be at "+" terminal of op-amp and V_2 must be at "-" terminal of op-amp.

→ M_1 & M_2 works as current source which will drive same current through both branches.

→ Now as we got a PTAT & CTAT quantities Voltage mode BGR we have to add PTAT & CTAT voltages. As we already have a CTAT Voltage we need to generate a PTAT voltage and this can be easily done by passing PTAT current through a resistor. So from simulation we can find slope of CTAT voltage and PTAT current and then accordingly decide the value of resistor. Let's say the value of resistor is R_2 . Thus our circuit will be,

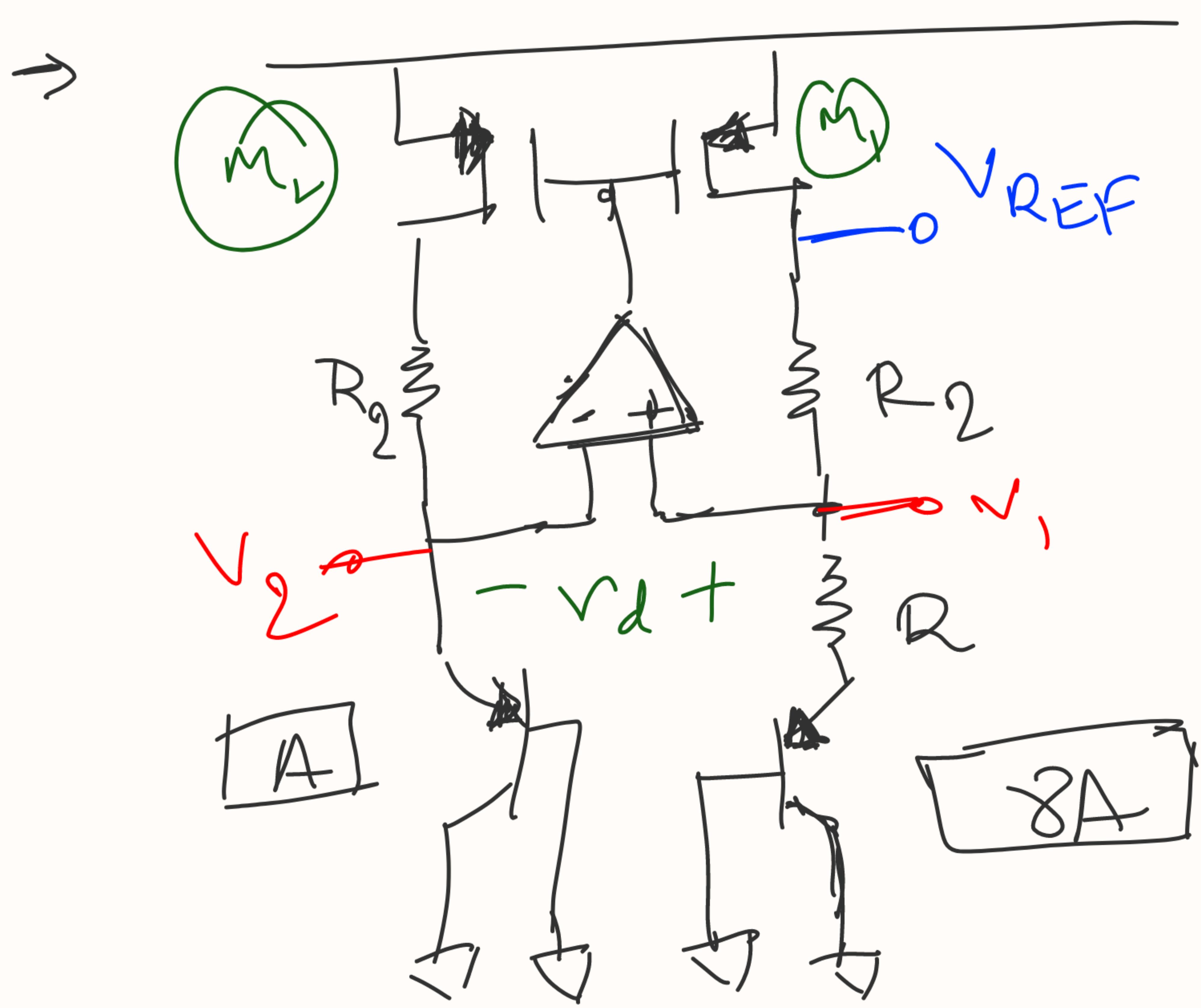

→ Note that we put R_2 on both the sides so that V_{sd} of both M_1 and M_2 are same and thus the difference in the currents of both the branches will be less.

(*) Design of Voltage Mode BGR

→ I selected the I_o of 5mA and the diode on Right branch has a multiplier of "8".

→ For $I_o = 5\text{mA}$, $I_o = V_T \frac{\ln(8)}{R}$, at room temperature $V_T = 25.9\text{mV}$ we get R as

$$R = \frac{25.9\text{mV} \times \ln(8)}{5\text{mA}} = 10.77\text{K}\Omega$$

→ For $M_1 \approx M_2$ we selected the lengths such that channel length modulation effect is minimum, so the current is almost same in both branches.


→ The size of M_1 & M_2 are

$$w_1 = w_2 = 10\text{ }\mu\text{m}$$


$$L_1 = L_2 = 1\text{ }\mu\text{m}$$



Schematic =

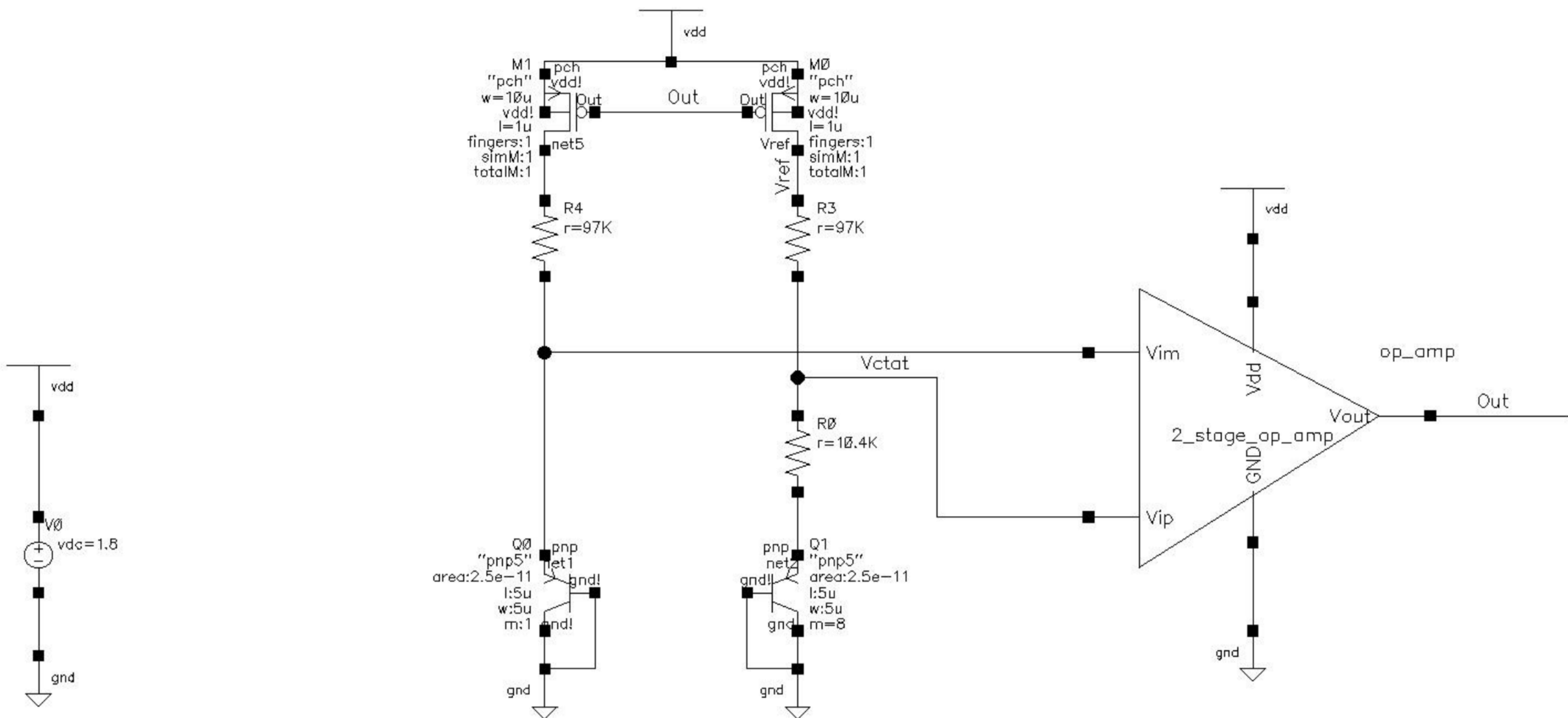

V_{Ctot} and I_{ptot} curves =

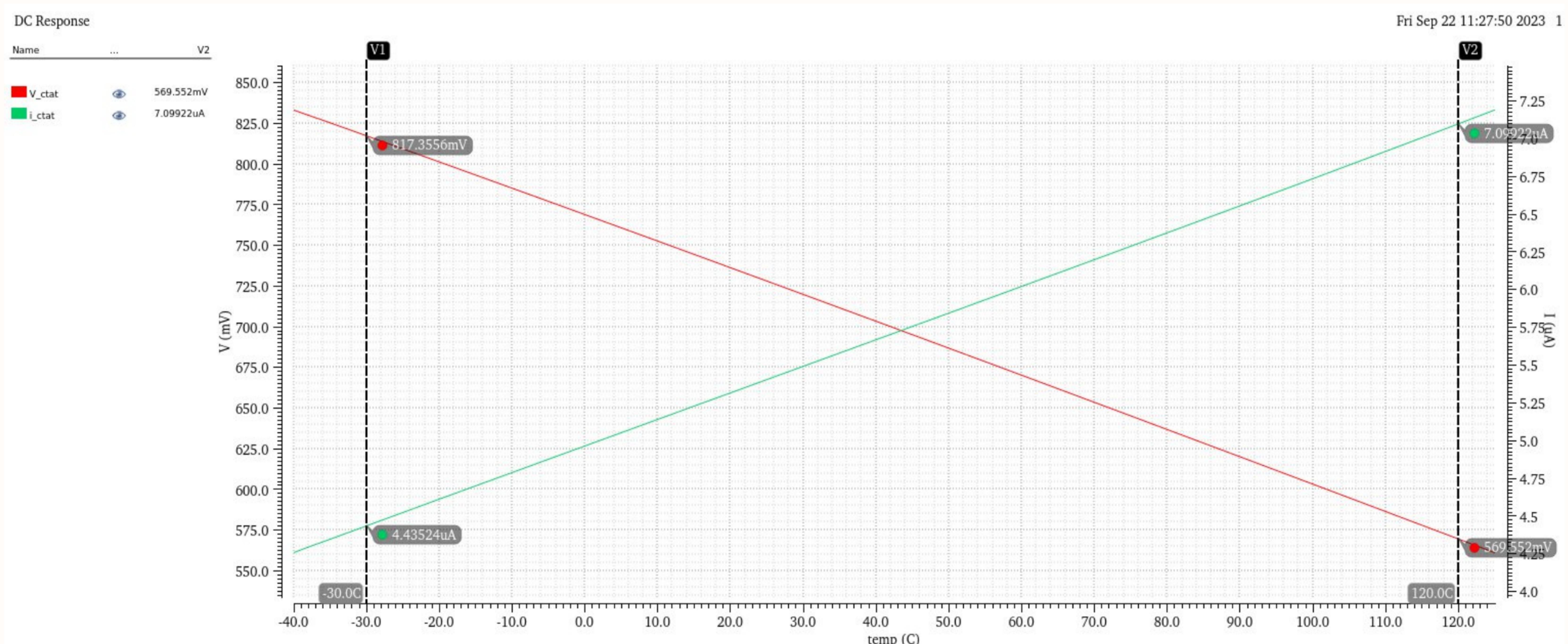

→ we varied the temperature from -40°C to 125°C and we found the slopes as,

$$V_{\text{ctat}} \text{ slope} = -1.652 \left(\frac{\text{mV}}{\text{C}} \right) \text{ and}$$

$$I_{\text{ptat}} \text{ slope} = 0.01776 \left(\frac{\mu\text{A}}{\text{C}} \right)$$


→ As we want a PTAT Voltage, thus

$$I_{\text{ptat}} \times R_2 = V_{\text{ctat}}$$

$$\therefore R_2 = 93.018 \text{ k}\Omega$$

→ But there can be a little deviation from our calculated value, thus we may do a parametric sweep, the result of parametric sweep is shown below.


\Rightarrow Parametric Sweep Result:

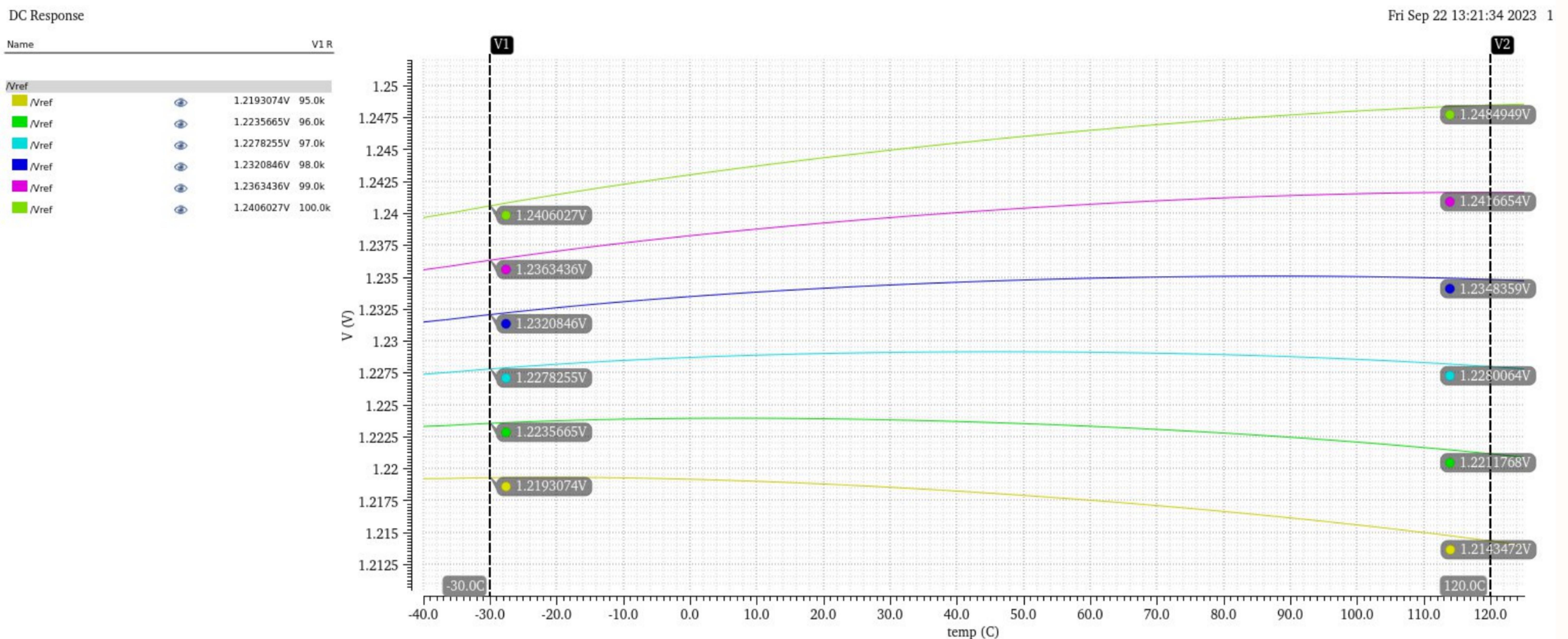

\rightarrow From graphs the curve corresponding to $97\text{ k}\Omega$ seems to have least variation along the temperature range.

\rightarrow Thus lets take $R_2 = 97\text{ k}\Omega$ and plot the curve of V_{ref} $\underline{\text{vs.}}$ Temp.

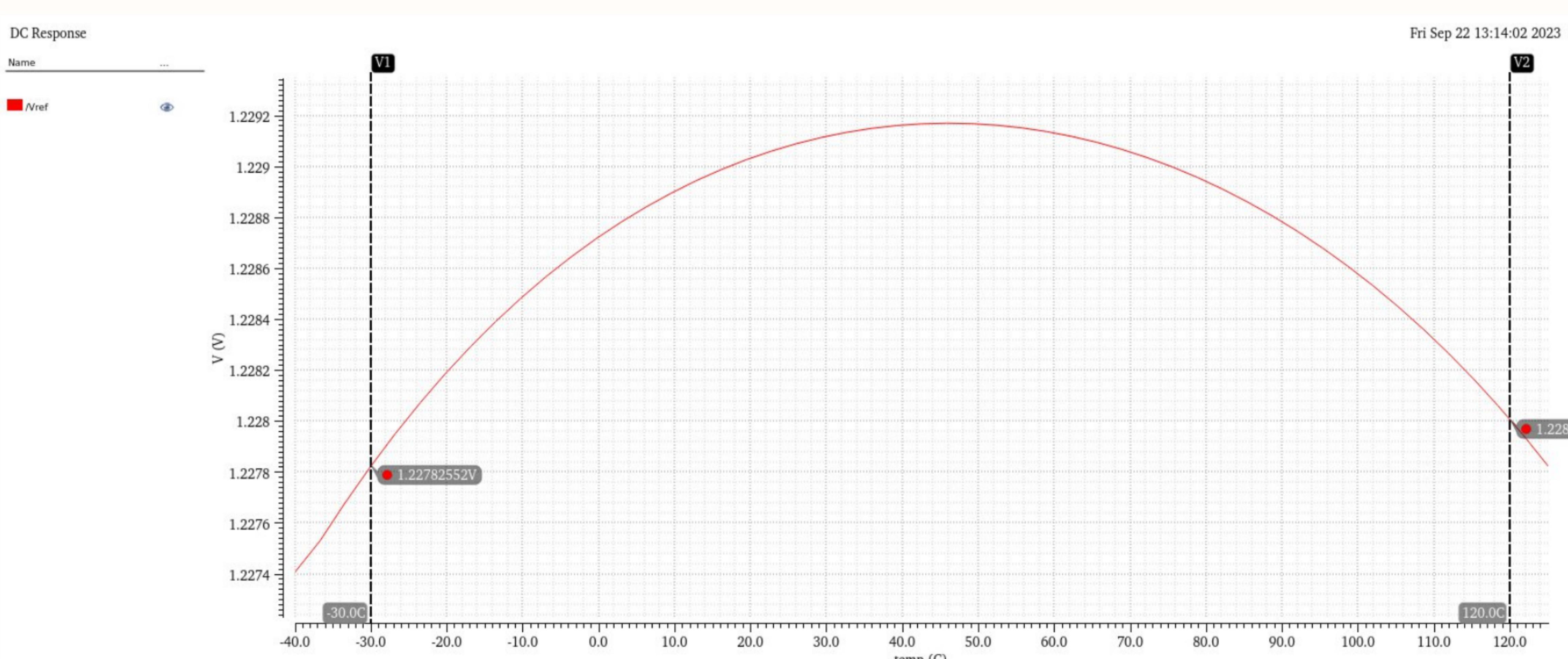\Rightarrow V_{ref} $\underline{\text{vs.}}$ Temp.




(*) Design of Current Mode BUR


⇒ Introduction

→ As we noticed from Voltage mode BCR the V_{ref} has value around 1.2 V which is coming due to bandgap of silicon. But as we are stacking voltages thus the supply voltage requirement is increased. Also if we need a reference voltage level other than 1.2 V then it is very difficult to get. Thus instead of stacking PTAT and CTAT voltages to get a temperature independent voltage we can add PTAT and CTAT currents to get a temperature independent current. As we already have a PTAT current, we just need a CTAT current. Now we have a CTAT voltage thus if we put a resistor across V_1 & V_2 , thus we get a CTAT current. And due to adding of resistor we are adding PTAT and CTAT currents thus current through M_1 & M_2 is temperature independent.

\Rightarrow Schematic:

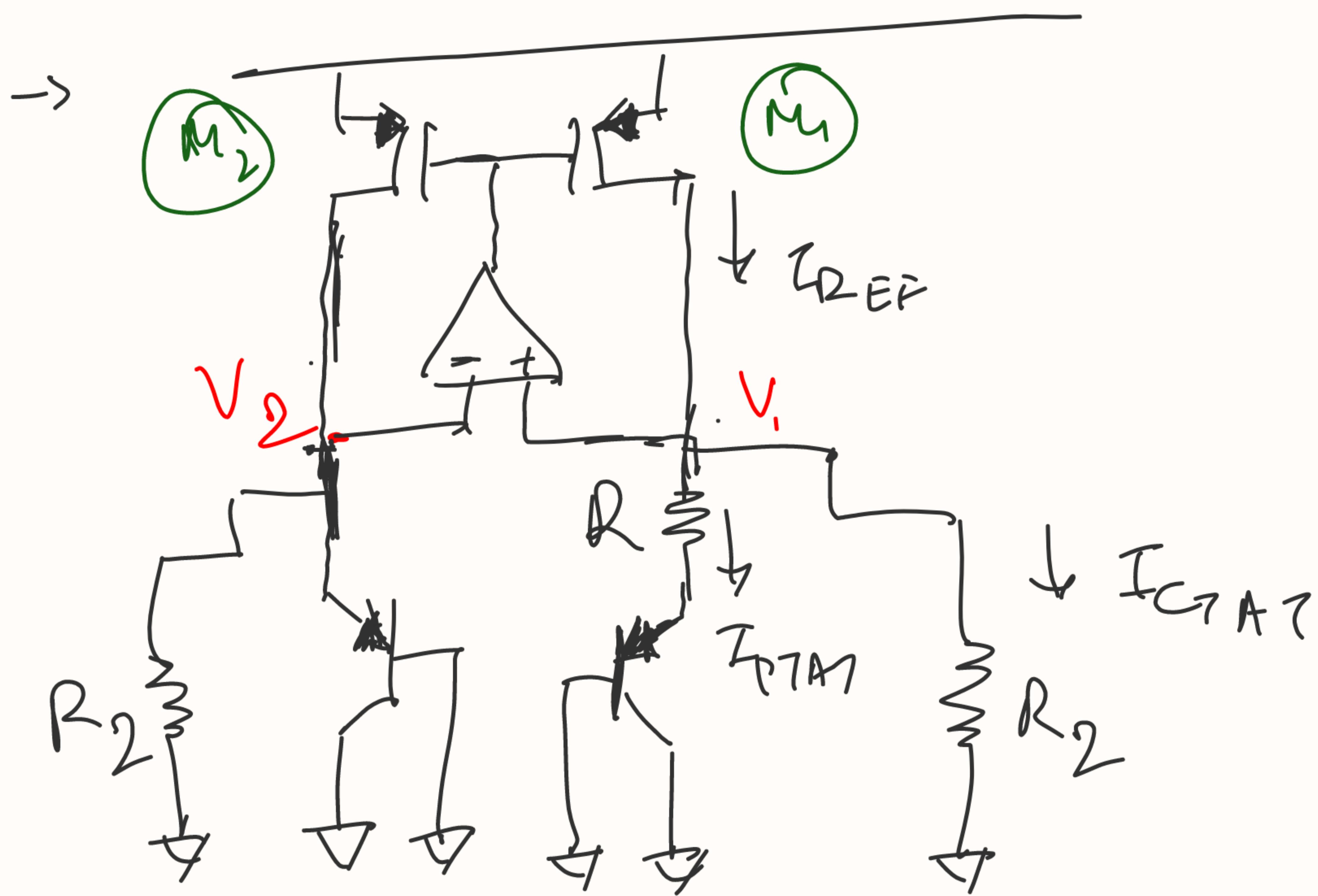


→ The value of R_2 is found from V_{CTAT} & I_{PTAT} slope values.
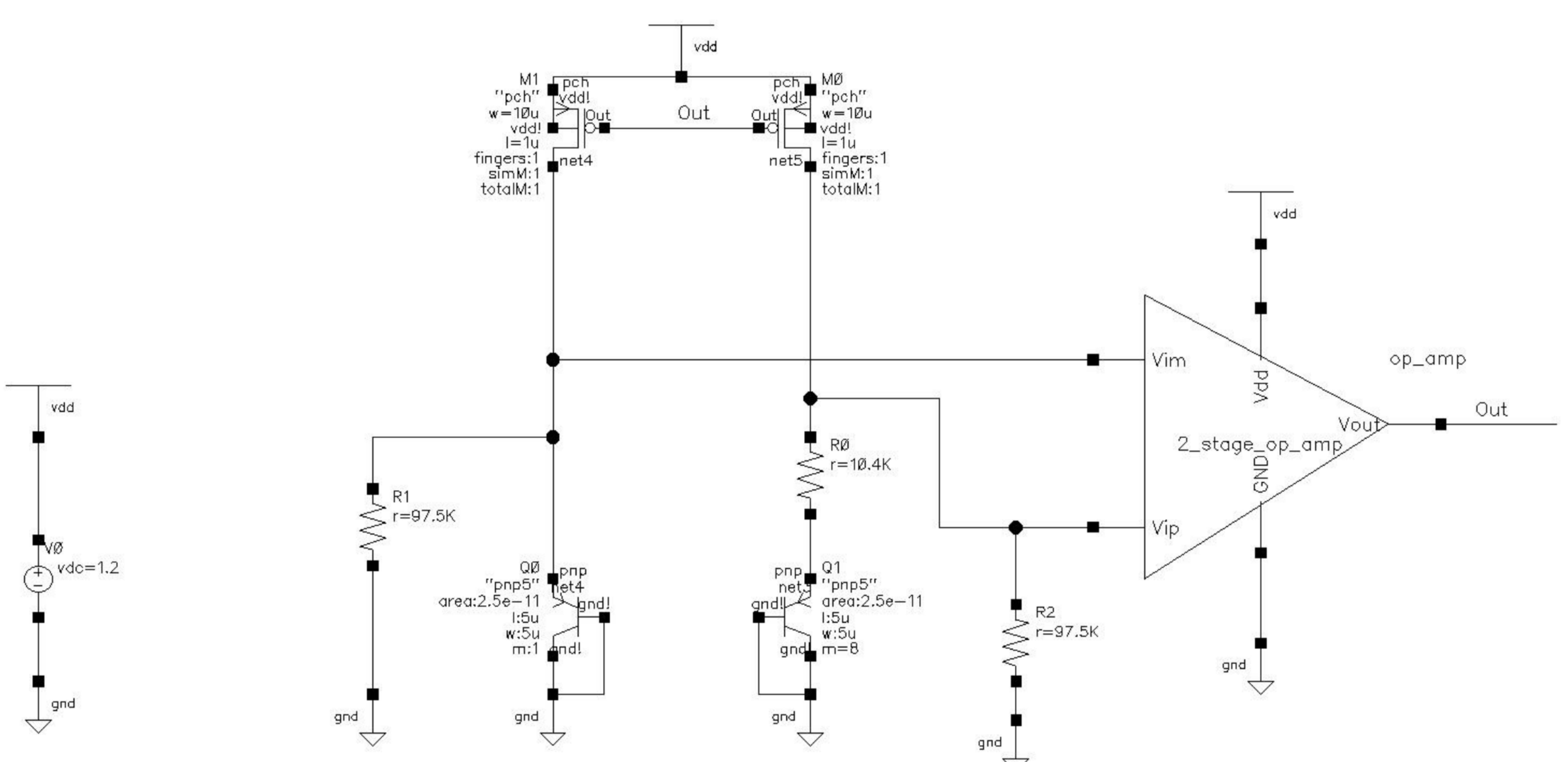
$$\frac{V_{CTAT}}{R_2} = I_{PTAT} \quad \Rightarrow \quad R_2 = \frac{1.652 \text{ (mV/c)}}{0.01776 \text{ (mA/c)}} = 93.018 \text{ k}\Omega$$


[SCHEMATIC]

→ But the actual value of R_2 may differ from 93.018 kΩ. Thus we will do parametric analysis for different values of R_2 around 93 kΩ.

→ Parametric sweep Results :-

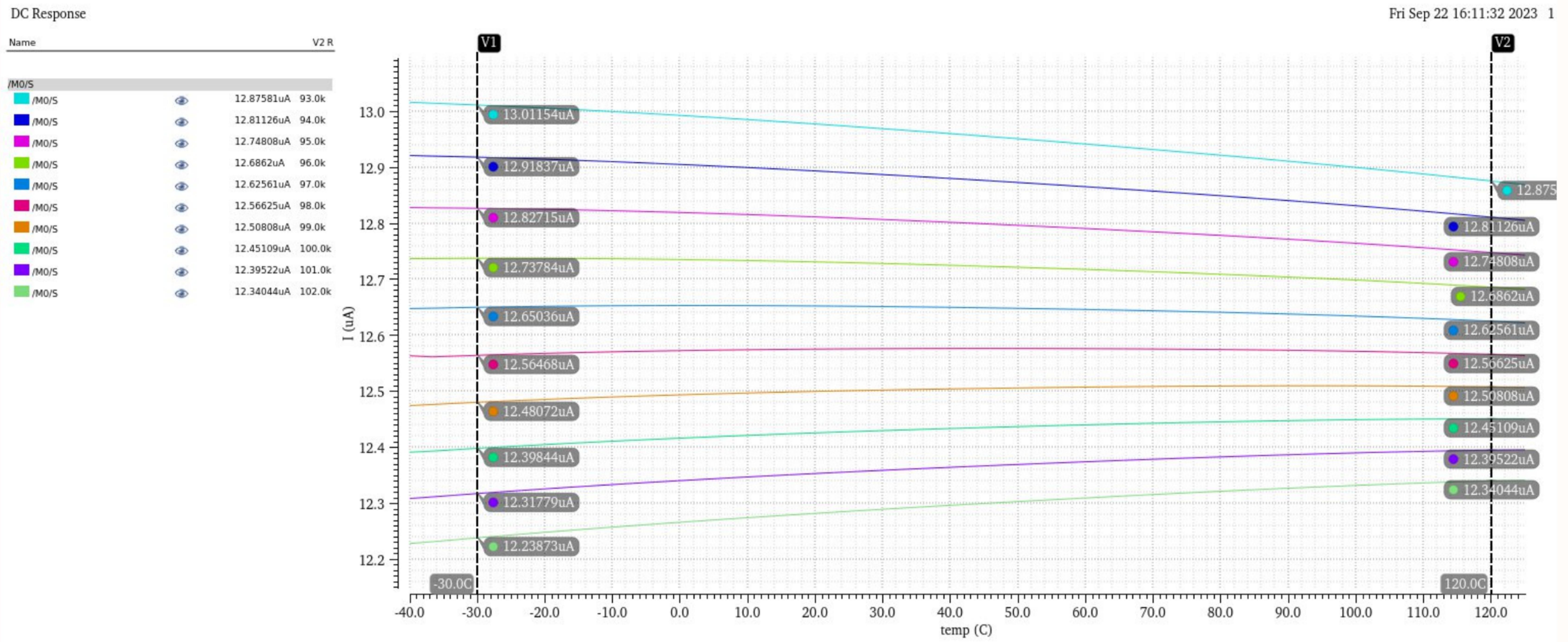

→ From this we selected $R_2 = 97.5\text{ k}\Omega$, for this the I_{REF} simulated result is as shown,

→ $I_{REF} \propto \text{Temperature}$.

